

Electrostatics and Circuits:

	<u>Variable</u>	<u>Unit</u>
	P	W
	V	V
	ΔU_e	J
	I	A
	R	Ω
	(constant) k	$N \cdot m^2/C^2$
	q or Q	C
	r	m
	d	m
	\overline{F}	N
electric field	\overline{E}	N/C
energy	E	J

Find all V's and I's:




$R_1 = 70 \Omega$

$R_2 = 90 \Omega$

$R_3 = 110 \Omega$

$R_4 = 85 \Omega$

$R_5 = 92 \Omega$

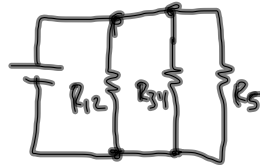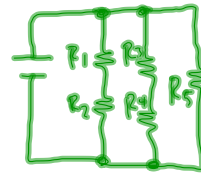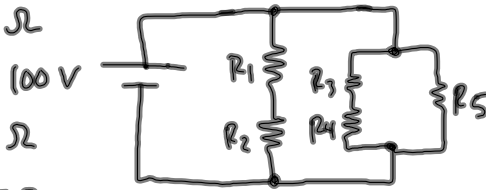

$R_{12} = 160 \Omega$


$R_{34} = 195 \Omega$



$\frac{1}{R_{eq}} = \frac{1}{R_{12}} + \frac{1}{R_{34}} + \frac{1}{R_5}$

$R_{eq} = 44.9 \Omega$

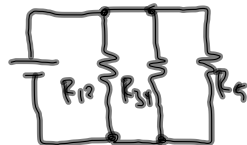
$I_{total} = \frac{V_{total}}{R_{eq}} = \frac{100V}{44.9\Omega} = 2.22 A$



$I_{12} = \frac{V_{total}}{R_{12}} = 0.625 A$

$I_{34} = \frac{V_{total}}{R_{34}} = 0.513 A$

$I_5 = \frac{V_{total}}{R_5} = 1.09 A$

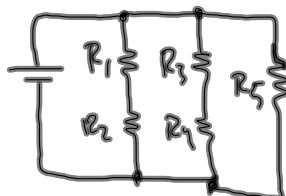


$V_1 = I_{12} R_1 = 44.7 V$

$V_2 = I_{12} R_2 = 56.3 V$

$V_3 = I_{34} R_3 = 56.4 V$


$V_4 = I_{34} R_4 = 43.6 V$

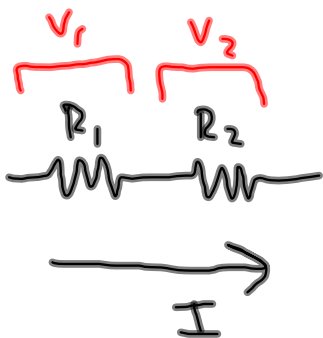

Series Connections:

Same I

Different V 's

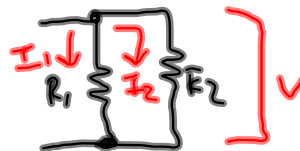

Parallel Connections:

Same V


Different I 's

Electrostatics and Circuits Review 4th Block 11.17.11

Three charges are arranged in a line. Charge 1 has a value of $-90 \mu\text{C}$ and is located at the origin, charge 2 has a value of $+80 \mu\text{C}$ and is located at $x = 2 \text{ cm}$, and charge 3 has a value of $-60 \mu\text{C}$ and is located at $x = 5 \text{ cm}$.

a) Find the value of the electric field at the point $x = 10 \text{ cm}$.

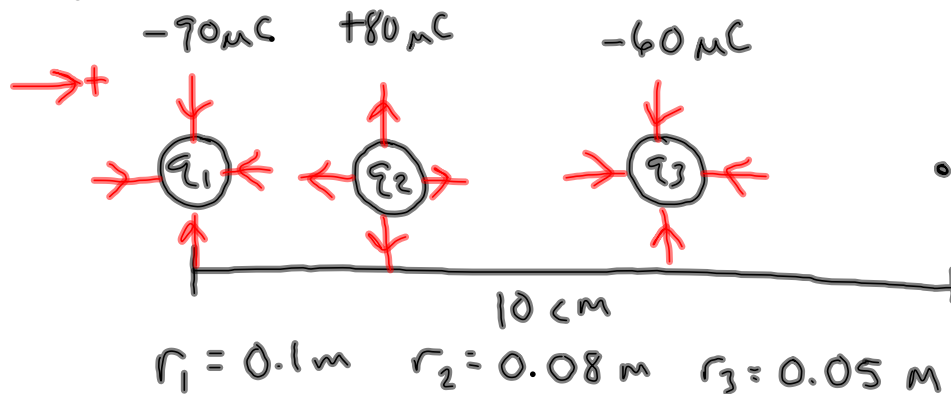b) If a charge of $+50 \mu\text{C}$ is placed at this point, what is the electric force that the charge experiences?



$$a) \bar{E}_{\text{net}} = \bar{E}_1 + \bar{E}_2 + \bar{E}_3$$

$$= k \left[\frac{-q_1}{r_1^2} + \frac{q_2}{r_2^2} + \frac{-q_3}{r_3^2} \right]$$


$$= (8.99 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2) \left[\frac{-(90 \times 10^{-6} \text{ C})}{(0.1 \text{ m})^2} + \frac{(80 \times 10^{-6} \text{ C})}{(0.08 \text{ m})^2} - \frac{(60 \times 10^{-6} \text{ C})}{(0.05 \text{ m})^2} \right]$$

$$= -1.84 \times 10^8 \text{ N/C}$$

$$b) \bar{E} = \frac{\bar{F}}{q}$$

$$\bar{F} = q \bar{E} = (+50 \times 10^{-6} \text{ C})(-1.84 \times 10^8 \text{ N/C})$$

$$= -9215 \text{ N}$$

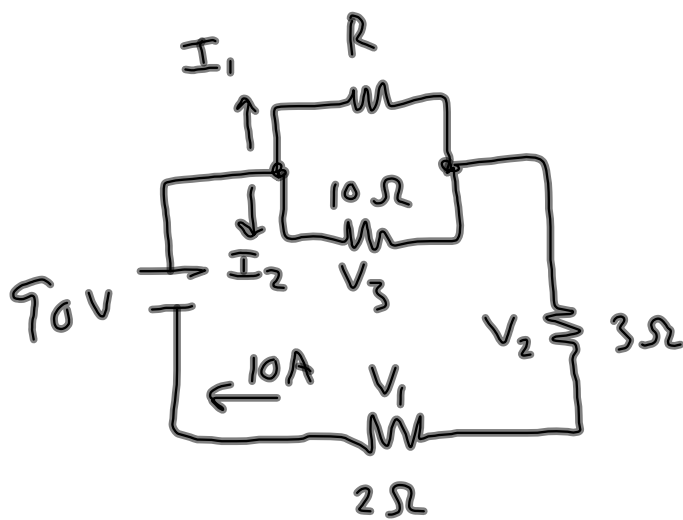

$$R = 6.67 \Omega$$

$$V_3 = 40 \text{ V}$$

$$V_2 = 30 \text{ V}$$

$$V_1 = 20 \text{ V}$$

$$I_1 = 6 \text{ A}$$

$$I_2 = 4 \text{ A}$$

$$I_{\text{total}} = 10 \text{ A}$$

$$I_2 = \frac{V_3}{10 \Omega} = 4 \text{ A}$$

$$V_1 = I_{\text{total}} (2 \Omega) = 20 \text{ V}$$

$$I_{\text{total}} = I_1 + I_2$$

$$V_2 = I_{\text{total}} (3 \Omega) = 30 \text{ V}$$

$$I_1 = 10 \text{ A} - 4 \text{ A} = 6 \text{ A}$$

$$V_{\text{total}} = V_1 + V_2 + V_3 \Rightarrow V_3 = 90 \text{ V} - 20 \text{ V} - 30 \text{ V} = 40 \text{ V}$$

$$R = \frac{V_3}{I_1} = \frac{40 \text{ V}}{6 \text{ A}} = 6.67 \Omega$$